

**EECE 144  
Fall 2011**

**Lab Report #3  
Section 4  
9/21/2011**

Submitted by:

Signature

Printed Name

Date

	<b>Jeremiah Mahler</b>	<b>Sep 21, 2011</b>
	<b>Marvane Johnson</b>	<b>Sep 21, 2011</b>

## **1 Description/Objectives**

The objective of this lab is to implement a logic function using actual hardware. The basic interfacing circuits using switches and outputs using LEDs are also introduced.

## **2 Procedure**


Equation 1 will be used as the logic function for this lab. The first step is to build a truth table definition (Figure 1). The next step is to implement the logic function using Logisim [1]. This will help as a guide for connecting hardware and can also be used to verify the truth table in Figure 1. The chips being used only have two inputs so the gates in Logisim should also use only two inputs.

$$ac + a'b + ab'c' \quad (1)$$

The inputs to the chips will be in the form of mechanical switches. If the switch is connected from the source voltage (5 volts) to the chip it will read the high value correctly but it will not read low correctly because the open circuit is not equivalent to low. To remedy this issue a pull down resistor is used to connect the pin at the chip to ground. A 1k resistor works well for this, larger values such as 10k may not work properly.

$ac + a'b + ab'c'$			
$a$	$b$	$c$	$z$ (out)
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	1

Figure 1: Truth table of outputs for the function  $ac + a'b + ab'c'$ .

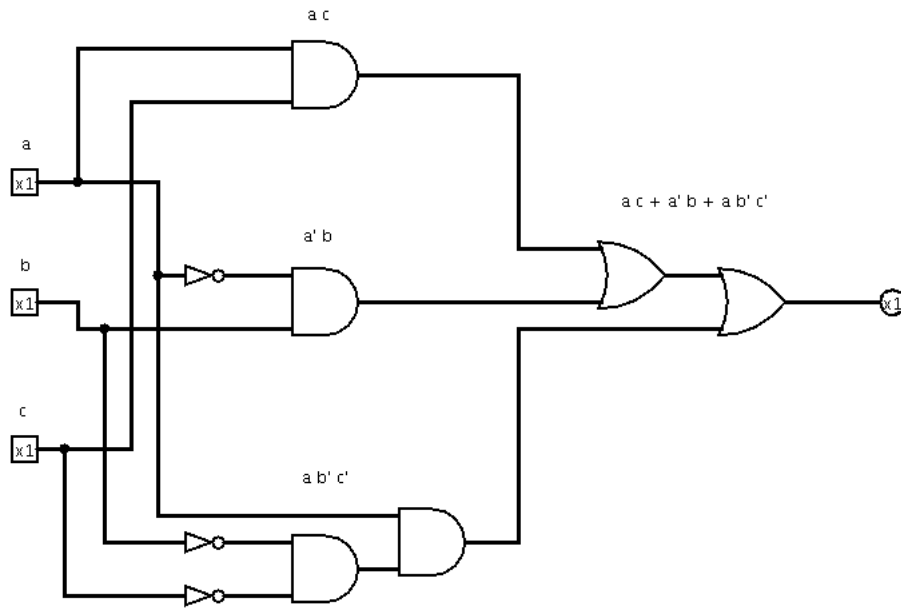

### **3 Observations**

### **4 Conclusion**

### **5 References**

- [1] Logisim, “Logisim, a graphical tool for designing and simulating logic circuits.” <http://ozark.hendrix.edu/~burch/logisim/>, 2011.