

**EECE 144**  
**Fall 2011**

**Lab Report #3**  
**Section 4**  
**9/21/2011**

Submitted by:

Signature

Printed Name

Date

	<b>Jeremiah Mahler</b>	<b>Sep 21, 2011</b>
	<b>Marvane Johnson</b>	<b>Sep 21, 2011</b>

**1 Description/Objectives**

**2 Procedure**

(Equations 1)

$$ac + a'b + ab'c' \quad (1)$$

$ac + a'b + ab'c'$			
$a$	$b$	$c$	z (out)
0	0	0	?
0	0	1	?
0	1	0	?
0	1	1	?
1	0	0	?
1	0	1	?
1	1	0	?
1	1	1	?

Figure 1: Truth table of outputs for the function  $ac + a'b + ab'c'$ .

### **3 Observations**

### **4 Conclusion**

### **5 References**

- [1] Logisim, “Logisim, a graphical tool for designing and simulating logic circuits.” <http://ozark.hendrix.edu/~burch/logisim/>, 2011.