

EECE 144
Fall 2011

Lab Report #7
Section 4
10/19/2011

Submitted by: Marvane Johnson

Signature	Printed Name	Date
	Jeremiah Mahler	Oct 19, 2011
	Marvane Johnson	Oct 19, 2011

1 Description/Objectives

The purpose of this lab is to find the min SOP expressions of equations J & K using a minimal amount of gates and to build a circuit combining the two equations using only two input gates. (Equation 1 and 2).

$$J(w, x, y, z) = \sum m(1, 3, 9, 11, 12, 13, 14, 15) \quad (1)$$

$$K(w, x, y, z) = \sum m(0, 1, 3, 12, 14) \quad (2)$$

2 Procedure

The first step in accomplishing this task was to create separate Karnaugh Map for expressions J & K in order to find the min SOPs of the equations and to determine the number of gates needed to implement each equation separately. The next step was to jointly optimize the two equations through the use of Karnaugh Maps to produce a circuit using the minimum number of gates. Lastly, we used the Truth table in order to test and verify the functionality of the circuit. (Table 1) The minimal SOP expression for J was found by the use of a Karnaugh Map. (Figure 1) (Equation 3).

$$J = wx + x'z \quad (3)$$

The minimal SOP expression for K was found by the use of a Karnaugh Map. (Figure 2) (Equation 4).

$$K = w'x'y' + w'x'z + wxz' \quad (4)$$

Figure 1 shows the Karnaugh map used for equation J in order to determine the number of gates and gate inputs needed. A total of 4 gates would be needed to implement expression

Index	w	x	y	z	J	K
0	0	0	0	0	0	1
1	0	0	0	1	1	1
2	0	0	1	0	0	0
3	0	0	1	1	1	1
4	0	1	0	0	0	0
5	0	1	0	1	0	0
6	0	1	1	0	0	0
7	0	1	1	1	0	0
8	1	0	0	0	0	0
9	1	0	0	1	1	0
10	1	0	1	0	0	0
11	1	0	1	1	1	0
12	1	1	0	0	1	1
13	1	1	0	1	1	0
14	1	1	1	0	1	1
15	1	1	1	1	1	0

Table 1: Truth table of functions J and K .

 


Figure 1: Karnaugh map of function J (Equation 1).

J ? (Figure 3) Figure 4 shows the Karnaugh map used for equation K in order to determine the number of gates and gate inputs needed. A total of 8 gates would be needed to implement expression J ? (Figure 4) TODO: What about the version K limited to 2 input gates? (Figure 5)

Diagram illustrating a 2D lattice structure with dimensions W , Y , and Z . The lattice is represented by a grid of values (0 or 1) indexed by coordinates (x, y) .

The grid values are:

0	1	5	4
2	3	7	6
10	11	15	14
8	9	13	12

The values in the grid are:

- Row 0: $[0, 1] = 1$, $[1, 5] = 1$, $[5, 4] = 0$, $[4, 3] = 0$
- Row 2: $[2, 3] = 0$, $[3, 7] = 1$, $[7, 6] = 0$, $[6, 6] = 0$
- Row 10: $[10, 11] = 0$, $[11, 15] = 0$, $[15, 14] = 0$, $[14, 3] = 1$
- Row 8: $[8, 9] = 0$, $[9, 13] = 0$, $[13, 12] = 0$, $[12, 3] = 1$

Figure 2: Karnaugh map of function K (Equation 2).

 


Figure 3: Circuit diagram of the minimal SOP solution of J .

 


Figure 4: Circuit diagram of the minimal SOP solution of K .

 


Figure 5: Circuit diagram of the minimal SOP solution of K when limited to two input gates.

A jointly optimized solution of J and K is created by combining shared term used by both SOP expressions of J and K . (Figure 6) (Equation 5)

$$\begin{aligned} J &= w'x'z + wxz' + wz \\ K &= w'x'z + wxz' + w'x'y' \end{aligned} \quad (5)$$

15 gates, and 7 inputs is the result of J and K joint solution (Figure 7). 4 NOT gates, 7

 


Figure 6: Jointly optimized Karnaugh maps for J and K .

AND gates and 4 OR gates were used to implement the J and K combined circuit. (Figure 7)

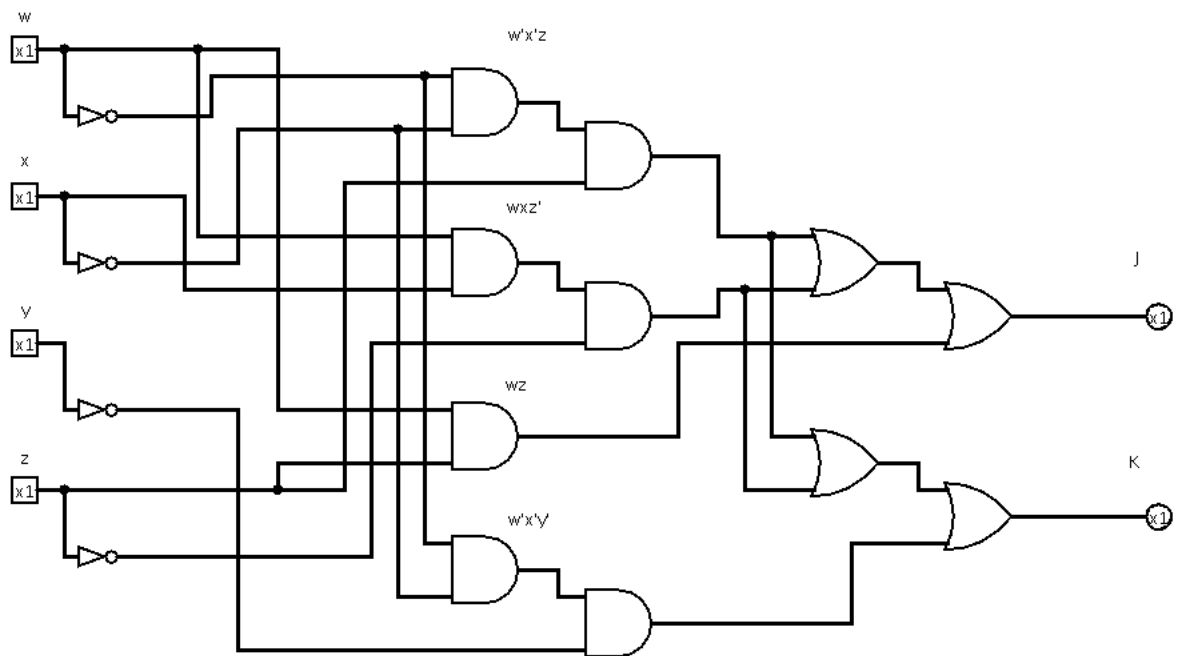


Figure 7: Circuit diagram of the jointly optimized solution of J and K when limited to two input gates.

3 Observations

The results of the implemented circuit in Figure 7 lines up with the Truth Table and produces the expected results.

<i>J</i> by itself			<i>J</i> and <i>K</i> independently		
gate type	# gates	# inputs	gate type	# gates	# inputs
AND	2	4	AND	8	16
OR	1	2	OR	3	6
NOT	1	1	NOT	5	5
TOTAL	4	7	TOTAL	16	27

<i>K</i> by itself, 2 input gates			<i>J</i> and <i>K</i> jointly		
gate type	# gates	# inputs	gate type	# gates	# inputs
AND	6	12	AND	7	14
OR	2	4	OR	4	8
NOT	4	4	NOT	4	4
TOTAL	12	20	TOTAL	15	26

Table 2: Metrics of gate and input counts for various configurations of *J* and *K*.

4 Conclusion

The lab was a success in demonstrating that shared hardware can be used to implement seperate expressions and still produce the desired outcome.