

**EECE 144**  
**Fall 2011**

**Lab Report #10**  
**Section 4**  
**11/9/2011**

Submitted by: Jeremiah Mahler

Signature

Printed Name

Date

	<b>Jeremiah Mahler</b>	<b>Nov 9, 2011</b>
	<b>Marvanee Johnson</b>	<b>Nov 9, 2011</b>

## 1 Description/Objectives

The objective of this lab is to design a three bit binary counter using at least one D flip-flop and at least one JK flip-flop. And then implement this design in hardware.

n	$Z_2$	$Z_1$	$Z_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1

Table 1: The sequence of states for a 3-bit binary counter where  $Z_0$  is the least significant bit. The counter should follow this order and when the end is reached it should loop to the beginning.

## 2 Procedure

The first step is to design the 3-bit counter. The strategy used here is to first solve the least significant bit and then proceed to the more significant bits. This is because the least significant bit does not depend on the state of any of the higher bits. The second bit depends on the state of the first bit. And the third bit depends on the state of the second and possibly the first.

Q	Q <sup>+</sup>	D
0	1	1
1	0	0

Table 2: States used to create a toggle using a D flip-flop.

Here we used one D flip-flop for the first bit and two JK flip-flops for subsequent bits. But other combinations are possible. In fact it is possible to use any register type for any bit position. It is even possible to implement a JK flip-flop out of a D flip-flop using only a few additional logic gates.

And after the design is created it will be implemented in hardware.

### 2.1 bit $Z_0$ , toggle using D flip-flop

The least significant bit behaves like a "toggle". When it is triggered by the clock it changes the output ( $Q^+$ ) to the opposite of its previous state ( $Q$ ).<sup>1</sup>

For the least significant bit,  $Z_0$ , the relevant states are given in Table 2. It can be seen that when  $Q$  is 0 we want the state,  $Q^+$ , to be 1. And the only way a D flip-flop can produce a 1 as an output is if it has a 1 on its input ( $D$ ). Similar reasoning can be used for the second row. To construct a function we need to decide what mapping from  $Q$  would produce the values in  $D$ . In this case it is simply  $D = Q'$ . What this function means in terms of the  $D$  flip-flop is that the output ( $Q'$ ) is connected to the input ( $D$ ). This is similar in design to a Johnson Counter.

### 2.2 bit $Z_1$ , using JK flip-flop

Bit  $Z_1$  is more complicated because it depends on the state of  $Z_0$ . Table 3 shows the relevant states for bit  $Z_1$ . Notice that the previous bit,  $Z_0$ , is included since it may depend on it. The value of  $Q^+$  is the desired value of  $Z_1$  during the next state given the current values of  $Z_0$  and  $Z_1$ . The values of each column of  $J$  and  $K$  are the values which will produce the desired value of  $Q^+$ .

To find a mapping between the input values of  $Z_0$  and  $Z_1$  to the output of  $J$  and  $K$ , Karnaugh Maps were used as shown in Figure 1. And this resulted in the equations  $J = Z_0$  and  $K = Z_0$ . Because they are both equal to  $Z_0$  this means that both the  $J$  and  $K$  inputs are connected together and to  $Z_0$ . And this will result in the desired output of  $Z_1$  on  $Q$  of this JK flip-flop.

---

<sup>1</sup>The notation used here denotes  $Q$  as the current state and  $Q^+$  as the next state.

(Q)		(Z <sub>1</sub> )						
Z <sub>1</sub>	Z <sub>0</sub>	Q <sup>+</sup>	J	K	J	K	J	K
0	0	0	0	0	0	1	0	X
0	1	1	1	1	1	0	1	X
1	0	1	0	0	1	0	X	0
1	1	0	1	1	0	1	X	1

Table 3: States used for the JK flip-flop of bit  $Z_1$ . The three columns of J K are equally valid solutions but the one containing "don't cares" (X) is the most general.

$J :$		$Z_0$	
		0	1
$Z_1$		X	X

$K :$		$Z_0$	
		X	X
$Z_1$		0	1

Figure 1: Karnaugh map for bit  $Z_1$  resulting in the equations  $J = Z_0$  and  $K = Z_0$ .

### 2.3 bit $Z_2$ , using JK flip-flop

Bit  $Z_2$  is the most complicated because it depends on the state of  $Z_0$  and  $Z_1$ . Table 4 shows the relevant states for bit  $Z_2$ .

The value of  $Q^+$  is the desired value of  $Z_2$  during the next state given the current values of  $Z_0$ ,  $Z_1$  and  $Z_2$ . The values of each column of  $J$  and  $K$  are the values which will produce the desired value of  $Q^+$ .

To find a mapping between the input values of  $Z_0$ ,  $Z_1$  and  $Z_2$  to the output of  $J$  and  $K$ , Karnaugh Maps were used as shown in Figure 2. And this resulted in the equations  $J = Z_1Z_0$  and  $K = Z_1Z_0$ . In this case the inputs to  $J$  and  $K$  are the same but they also involve an AND gate of  $Z_1$  and  $Z_0$  before entering  $J$  and  $K$ . And this will result in the

$(Q)$		$(Z_2)$							
$Z_2$	$Z_1$	$Z_0$	$Q^+$	J	K	J	K	J	K
0	0	0	0	0	0	0	1	0	X
0	0	1	0	0	0	0	1	0	X
0	1	0	0	0	0	0	1	0	X
0	1	1	1	1	1	1	0	1	X
1	0	0	1	0	0	1	0	X	0
1	0	1	1	0	0	1	0	X	0
1	1	0	1	0	0	1	0	X	0
1	1	1	0	1	1	0	1	X	1

Table 4: States used for the JK flip-flop of bit  $Z_2$ .

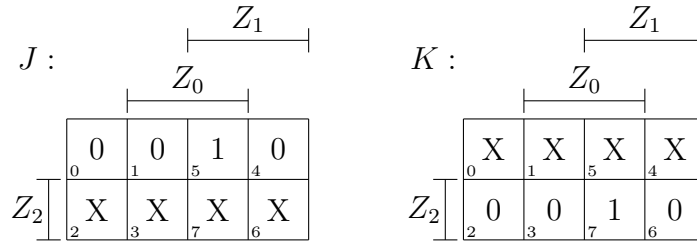


Figure 2: Karnaugh map for bit  $Z_2$  resulting in the equations  $J = Z_1Z_0$  and  $K = Z_1Z_0$ .

 


Figure 3: A 3 bit counter using 1 D flip-flop and 2 JK flip-flops with bit  $Z_0$  as the least significant bit.

desired output of  $Z_2$  on  $Q$  of this JK flip-flop.

## 2.4 Implementation in hardware

Combining the design for each individual bit results in the circuit shown in Figure 3.

To implement this design the circuit diagram should be followed along with the relevant data sheets for the particular chips.

The following four chips were used during the construction of this lab.

74HC74	dual D flip-flop
74HC109	dual JK flip-flop
74HC08	quad 2 input and gates
74HC04	hex inverting gates

Other chips can be substituted but they must all be from the same family. CMOS chips cannot be mixed with TTL chips.

On the flip-flops there are additional pins for "reset" and "clear". These are used to momentarily reset and/or clear the state of the chip. But in this lab it was not necessary to use them so they were just connected to hi or low (refer to the data sheet).

The clock inputs to all the chips was the same and was derived from a switch. It could also be derived from a function generator. If a function generator is used the frequency should be reduced to a value such as 1 hz so that it does not change too fast to be seen.

### **3 Observations**

The 3 bit counter implemented in hardware sequentially counted from 0 to 7 as expected. On power up the initial state was not always the same. This was not a problem in this case since all possibilities were accounted for but it could be a problem in other situations. The reset and clear pins could also be used to reset the state if this was necessary.

### **4 Conclusion**

This lab was a success in designing and implementing a 3-bit binary counter using D and JK flip-flops.