

Lab 13

Sequential Taillights

Lab report due before your lab period on December 7–9
Demo before the end of lab December 7–9

- Read the description for Problem 16.27
- Use Verilog to write a module that controls the sequential taillights
 - Your Verilog module must have the following format

```
module taillights(input clk, L, R, H, output reg [2:0] TL, TR);
endmodule
```
 - When L=1, the output TL cycles through the sequence: 3'000, 3'b001, 3'b011, 3'b111, 3'b000, etc.
 - When R=1, the output TR cycles through the sequence: 3'000, 3'b100, 3'b110, 3'b111, 3'b000, etc.
- Demonstrate your implementation to your TA

The report for this lab should include the following sections:

1. Description/Objectives
2. Procedure
3. Observations
4. Conclusions
5. Appendix
 - (a) The Verilog code for your implementation (not your testbench)