

EECE 144
Fall 2011

Lab Report #7
Section 4
10/19/2011

Submitted by: Marvane Johnson

Signature	Printed Name	Date
	Jeremiah Mahler	Oct 19, 2011
	Marvane Johnson	Oct 19, 2011

1 Description/Objectives

TODO: What is the objective of this lab? (Equation 1 and 2).

$$J(w, x, y, z) = \sum m(1, 3, 9, 11, 12, 13, 14, 15) \quad (1)$$

$$K(w, x, y, z) = \sum m(0, 1, 3, 12, 14) \quad (2)$$

2 Procedure

TODO: Describe the procedure used to complete this lab. What analysis techniques are used (e.g. Karnaugh Maps). What was calculated?

(Table 1)

TODO: Describe how the minimal SOP expression for J was found. (Figure 1) (Equation 3).

$$J = wx + x'z \quad (3)$$

TODO: Describe how the minimal SOP expression for K was found. (Figure 2) (Equation 4).

$$K = w'x'y' + w'x'z + wxz' \quad (4)$$

Index	w	x	y	z	J	K
0	0	0	0	0	0	1
1	0	0	0	1	1	1
2	0	0	1	0	0	0
3	0	0	1	1	1	1
4	0	1	0	0	0	0
5	0	1	0	1	0	0
6	0	1	1	0	0	0
7	0	1	1	1	0	0
8	1	0	0	0	0	0
9	1	0	0	1	1	0
10	1	0	1	0	0	0
11	1	0	1	1	1	0
12	1	1	0	0	1	1
13	1	1	0	1	1	0
14	1	1	1	0	1	1
15	1	1	1	1	1	0

Table 1: Truth table of functions J and K .

 


Figure 1: Karnaugh map of function J (Equation 1).

TODO: How are the number of gates and gate inputs determined? What are these counts for expression J ? (Figure 3)

TODO: Similar to J , how is this done for K ? (Figure 4)

TODO: What about the version K limited to 2 input gates? (Figure 5)

$$K(w, x, y, z):$$

				x	
				z	
y	w	0	1	1	0
		1	1	5	4
	2	0	1	7	6
	3	0	1	0	0
w	10	0	0	0	1
	11	0	0	15	14
	8	0	0	0	1
	9	0	0	13	12

Figure 2: Karnaugh map of function K (Equation 2).

 


Figure 3: Circuit diagram of the minimal SOP solution of J .

 


Figure 4: Circuit diagram of the minimal SOP solution of K .

 


Figure 5: Circuit diagram of the minimal SOP solution of K when limited to two input gates.

TODO: What about for the jointly optimized solution of J and K ? (Figure 6) (Equation 5)

$$\begin{aligned} J &= w'x'z + wxz' + wz \\ K &= w'x'z + wxz' + w'x'y' \end{aligned} \quad (5)$$

 


Figure 6: Jointly optimized Karnaugh maps for J and K .

TODO: How many gates, how many inputs for the joint solution? (Figure 7).

TODO: describe the hardware implementation. (Figure 7)

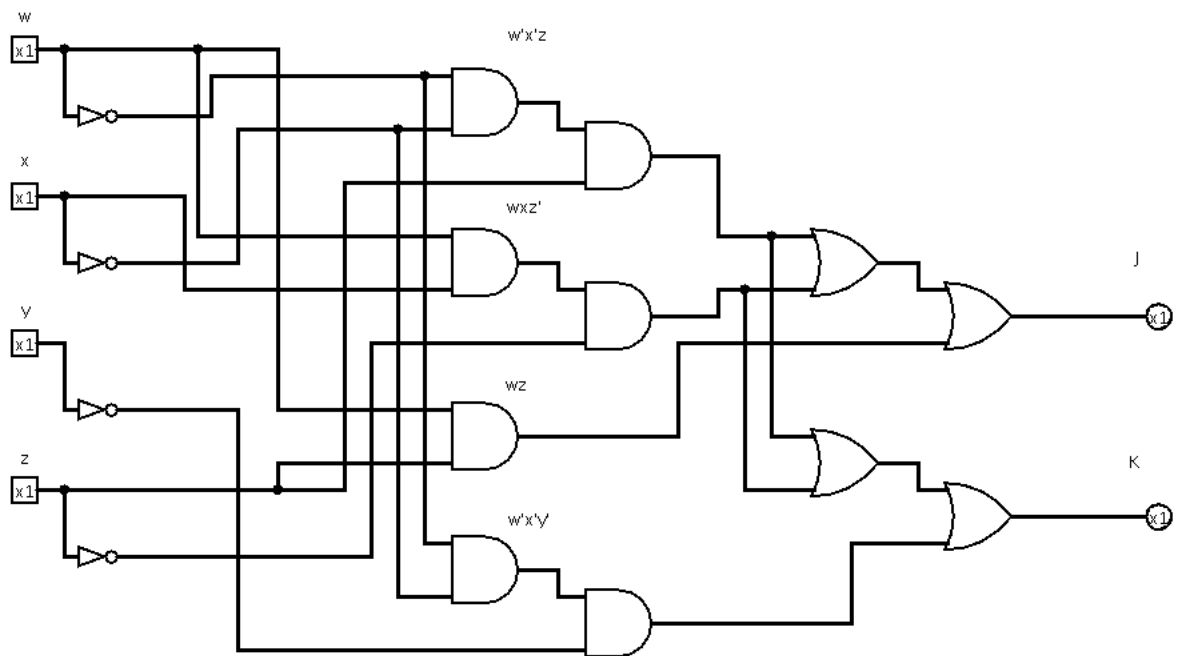


Figure 7: Circuit diagram of the jointly optimized solution of J and K when limited to two input gates.

3 Observations

TODO: How do the counts of various implementations compare? Does the resulting function match the truth table?

<i>J</i> by itself			<i>J</i> and <i>K</i> independently		
gate type	# gates	# inputs	gate type	# gates	# inputs
AND	2	4	AND	8	16
OR	1	2	OR	3	6
NOT	1	1	NOT	5	5
TOTAL	4	7	TOTAL	16	27

<i>K</i> by itself, 2 input gates			<i>J</i> and <i>K</i> jointly		
gate type	# gates	# inputs	gate type	# gates	# inputs
AND	6	12	AND	7	14
OR	2	4	OR	4	8
NOT	4	4	NOT	4	4
TOTAL	12	20	TOTAL	15	26

Table 2: Metrics of gate and input counts for various configurations of *J* and *K*.

4 Conclusion

TODO: Was this lab a success in achieving the objective?