

## Lab 5

### Karnaugh Map Reduction

Due before your lab period on October 5–7

- Determine the canonical SOP equation for  $f$

$$f(a, b, c) = \sum m(0, 2, 3, 4, 6)$$

- Generate the truth table for  $f$
- Determine the number of gates required to implement the canonical SOP equation for  $f$ . Gates can have any number of inputs.
- Simplify  $f$  using a Karnaugh Map and generate the simplified equation
- Implement the simplified version of  $f$  using ICs and verify it using your truth table
  - Use only the 7408, 7432, and 7404 ICs
  - Use switches for inputs and the bar LEDs as outputs
- Demonstrate your circuit to your lab TA

The report for this lab should include the following sections:

1. Description/Objectives
2. Procedure, which must include
  - (a) Canonical SOP equation for  $f$
  - (b) Truth table for  $f$
  - (c) Karnaugh Map reduction of  $f$
3. Observations
4. Conclusions