

Lab 10

Binary Counter

Lab report due in OCNL 318 by 5 PM on November 10

- Design a three-bit binary counter
 - The counter follows the sequence $000 \rightarrow 001 \rightarrow 010 \dots 110 \rightarrow 111 \rightarrow 000$ and repeats
 - You must use at least one JK flip-flop and at least one D flip-flop
 - Do not use the 74HC193 IC
- Use a function generator or switch as a clock input
- Build your circuit and verify its operation using a state table
- Demonstrate your circuit to your TA

The report for this lab should include the following sections:

1. Description/Objectives
2. Procedure, which must include
 - (a) The input equations for every flip-flop
 - (b) Circuit diagram for the counter
 - (c) The state table you used to test your implementation
3. Observations
4. Conclusions